
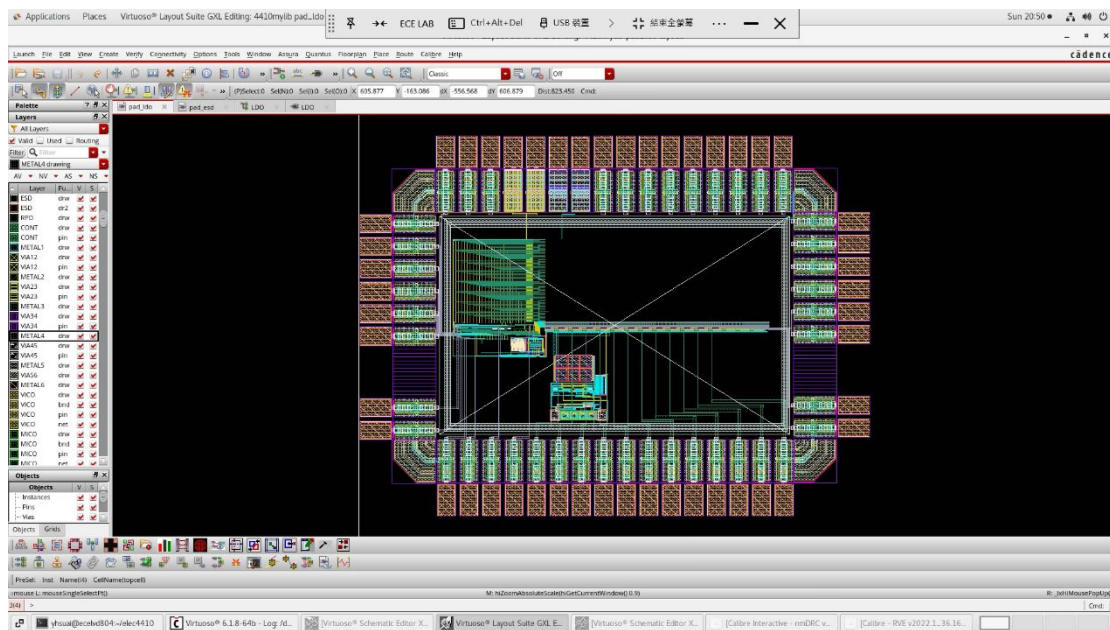


B

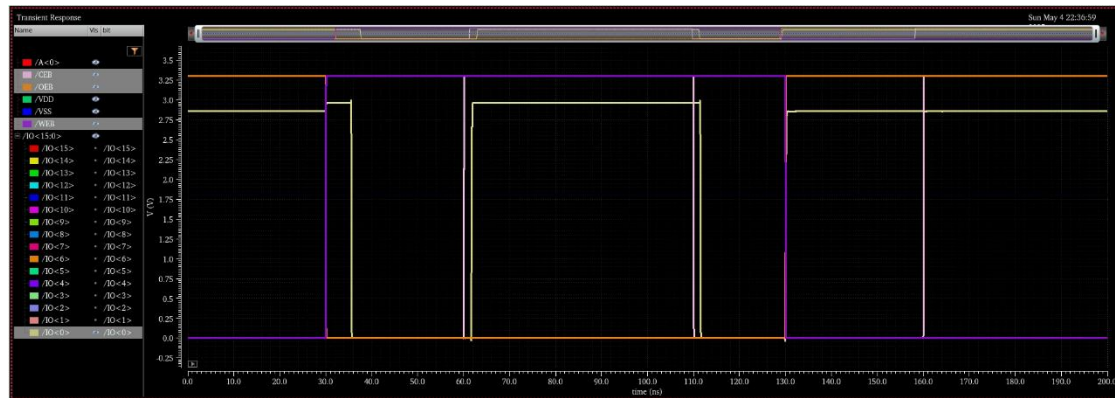

C



The i/o pad is initial to be 3.3V, I have use a transmission gate to make sure the initial data won't go in pad during read so the IO<0> didn't go to 3.3, the delay is about 32ns